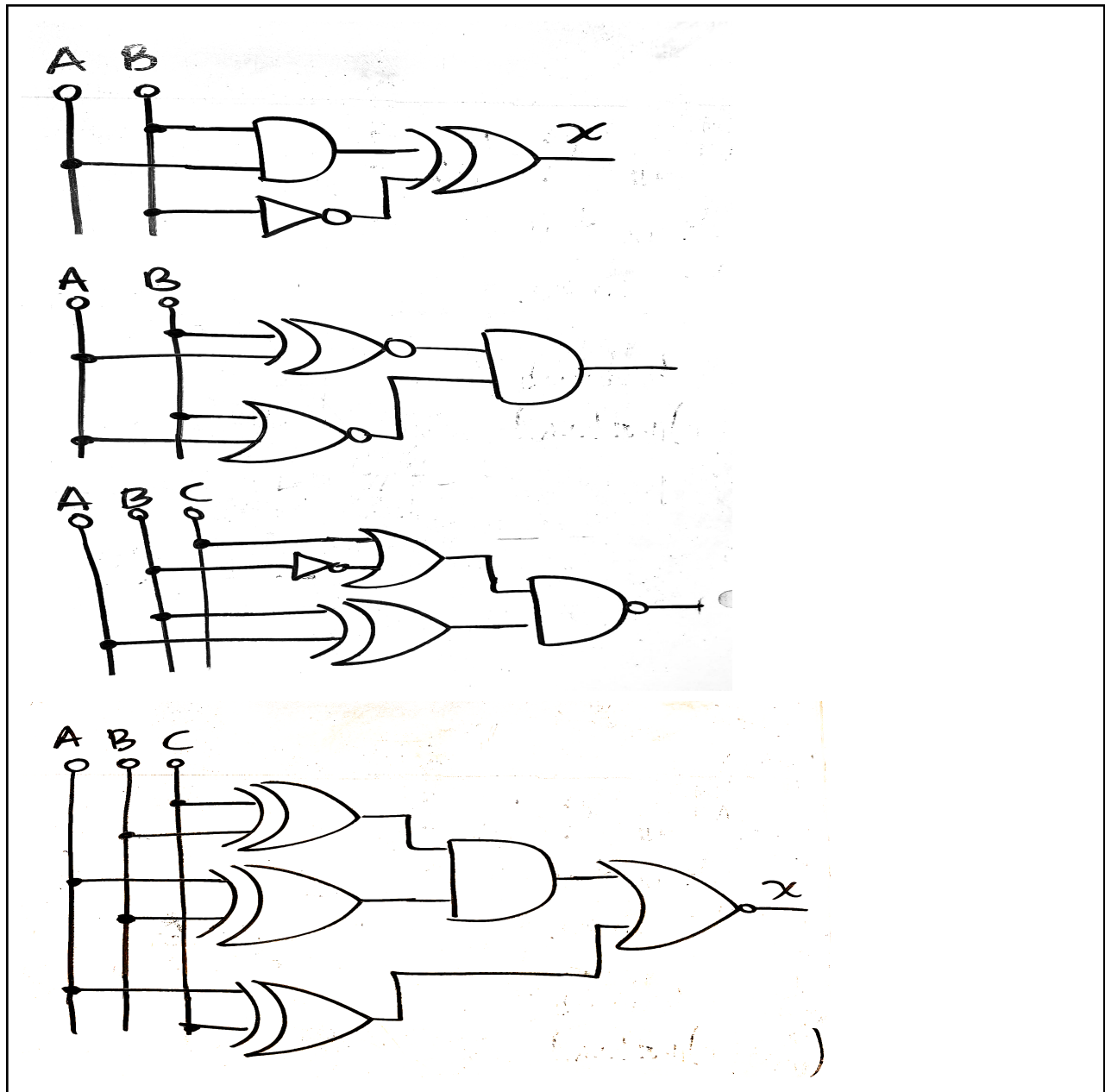


① Write the logic equation for the diagrams below:



② Draw the diagram for the logic equations below:

1.  $\text{Out1} = A + C + BD + (\text{not}B \text{ not}D)$
2.  $\text{Out2} = \text{not}B + (\text{not}C \text{ not}D) + CD$
3.  $\text{Out3} = B + \text{not}C + D$
4.  $\text{Out4} = (\text{not}B \text{ not}D) + (C \text{ not}D) + (BC\text{not}D) + (\text{not}B C) + A$

③ Simplify the K-map Tables below and write the logical equations:

**Table 1**

ab/ c	00	01	11	10
0		1		
1		1	1	

**Table 2**

ab/ c	00	01	11	10
0		1		1
1		1	1	1

**Table 3**

ab/ c	00	01	11	10
0	1			1
1	1			1

**Table 4**

ab/ c	00	01	11	10
0	1	1	1	1
1			1	

**Table 1**

ab/ cd	00	01	11	10
00	1			1
01				
11				
10	1			1

- ④ The apartment below needs a notification system that sends an SMS to the owner when:
- Any of the two windows is open when the main door is locked,
  - The baranda's door is open when the main door is locked,
  - The TV screen is ON when the washing machine and the dish washing machine are ON.

Add 2 more rules and find the equation for the notification system.

